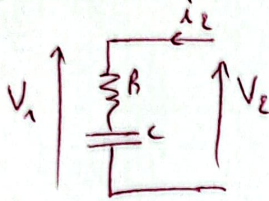


# Ex 1:

1) The impedance matrix:


\* Suppose that  $i_1 = 0$ :



$$V_1 = V_2 = \left( R + \frac{1}{j\omega C} \right) i_2$$

$$Z_{12} = \frac{V_1}{i_2} \Big|_{i_1=0} \quad Z_{22} = \frac{V_2}{i_2} \Big|_{i_1=0}$$

\* Suppose that  $i_2 = 0$ :

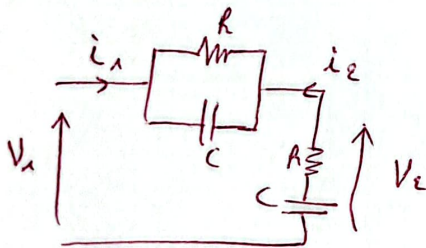

$$V_1 = \left[ \left( j\omega C + \frac{1}{R} \right)^{-1} + R + \frac{1}{j\omega C} \right] i_1$$

$$V_2 = \left( R + \frac{1}{j\omega C} \right) i_2$$


$$Z_{11} = \frac{V_1}{i_1} \Big|_{i_2=0} \quad Z_{21} = \frac{V_2}{i_1} \Big|_{i_2=0}$$

$$\Rightarrow Z = \begin{bmatrix} \frac{R}{1+j\omega RC} + R + \frac{1}{j\omega C} & R + \frac{1}{j\omega C} \\ R + \frac{1}{j\omega C} & R + \frac{1}{j\omega C} \end{bmatrix}$$

(0,5)      (0,5)      (0,5)      (0,5)

2) The hybrid matrix:


\* Suppose that  $i_1 = 0$ :

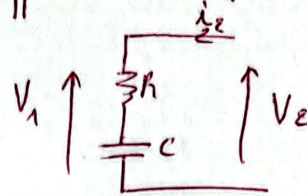

$$V_1 = V_2 = \left( R + \frac{1}{j\omega C} \right) i_2$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{i_1=0} \quad h_{22} = \frac{i_2}{V_2} \Big|_{i_1=0}$$

\* Suppose that  $V_2 = 0$ :

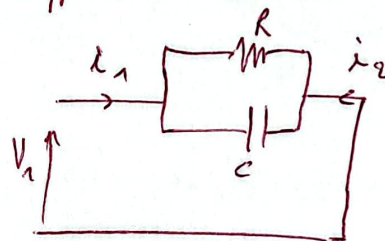

$$i_1 = -i_2$$


$$V_1 = \left( j\omega C + \frac{1}{R} \right)^{-1} i_1$$

$$h_{11} = \frac{V_1}{i_1} \Big|_{V_2=0} \quad h_{21} = \frac{i_2}{i_1} \Big|_{V_2=0}$$

$$\Rightarrow H = \begin{bmatrix} \frac{R}{1+j\omega RC} & 1 \\ -1 & \frac{j\omega C}{1+j\omega RC} \end{bmatrix}$$

(2)

3)

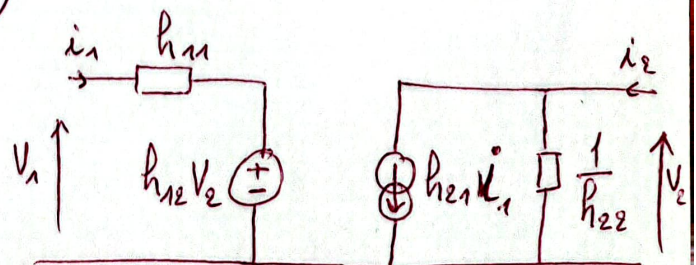

(1,5)

4) The voltage gain:

We have:

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

$$\Rightarrow i_1 = \frac{1}{h_{21}} i_2 - \frac{h_{22}}{h_{21}} V_2$$

$$\text{We know that: } V_2 = -R_L i_2 \Rightarrow i_2 = -\frac{V_2}{R_L}$$

$$\Rightarrow V_{r1} = -\frac{h_{11}}{h_{21}} \frac{V_2}{R_L} - \frac{h_{11} h_{22}}{h_{21}} V_2 + h_{12} V_2$$

$$\frac{V_2}{V_1} = \frac{h_{21} R_L}{h_{12} h_{21} R_L - h_{11} h_{22} R_L - h_{11}}$$

(2)

$$\frac{V_2}{V_1} = \frac{Z_{21} R_L}{R_L Z_{11} + Z_{11} Z_{22} - Z_{12} Z_{21}}$$

$$\frac{V_2}{V_1} = \frac{Z_B R_L}{Z_A R_L + Z_A Z_B + Z_B R_L}$$

$$Z_A = \frac{R}{1 + j\omega R C}$$

$$Z_B = R + \frac{1}{j\omega C}$$