

# Retake Exam Solution

## \* Problem:

0,5


1) The design C is different from A with only resistance  $R_6 = 954 \Omega$ , it is clear that

C is the approximation and (A, B) are the equivalent circuits. 0,5

Justification: apply Thevenin to circuit B

we obtain

with  $R_{th} = R_1 \parallel R_2$

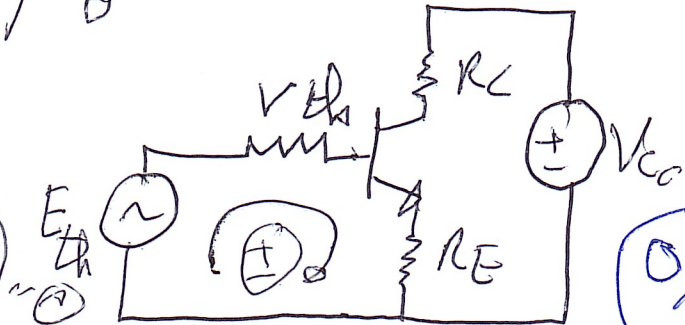

0,5

and  $E_{th} = \frac{R_1}{R_1 + R_2} V_{CC}$  ... ②

\* Validity of the approximation:

1) (I)  $\Rightarrow E_{th} - V_{th} I_B - R_E I_E - V_{BE} = 0$

$$\Rightarrow -I_E \left( R_E + \frac{V_{th}}{\beta} \right) + (E_{th} - V_{BE}) = 0$$

0,5

$$I_E = \frac{E_{th} - V_{BE}}{R_E + \frac{V_{th}}{\beta}} \quad \dots (3)$$

from Design A (3)  $\Rightarrow I_E = \frac{V_{DD} - V_{BE}}{R_E + \frac{R_1 \parallel R_2}{\beta}}$

(1 / 5)

Using Approximation we got

$$V_{BB} - R_E I_E' - V_{BE} = 0 \Rightarrow I_E' = \frac{V_{BB} - V_{BE}}{R_E}$$

$$I_E' \approx I_E \text{ if } \frac{(R_1 \parallel R_2)}{\beta} \ll R_E$$

$$\Rightarrow (R_1 \parallel R_2) \ll \beta R_E \quad ((R_1 \parallel R_2) = R_b)$$

e) Easiest circuit to me is A:

$$I_{E_0} = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_1 \parallel R_2}{\beta}} = \frac{3,22 - 0,7}{2,2 \cdot 10^3 + \frac{R_b}{213}} = \frac{2,52}{\dots} = 1,14 \text{ mA}$$

$$\text{AND } V_{CC} - V_{CE_0} - (R_C + R_E) I_E = 0$$

$$\Rightarrow V_{CE_0} = V_{CC} - (R_C + R_E) I_E$$

$$V_{CE_0} = 4,59 \text{ volts}$$

$$\left\{ \begin{array}{l} R_1 \parallel R_2 = R_b = 964 \Omega \\ \frac{R_1 V_{CC}}{R_1 + R_2} = 3,22 \text{ volts} \end{array} \right\} \Rightarrow \frac{R_1 \cdot R_2}{R_1 + R_2} = R_b$$

$$\frac{R_1}{R_1 + R_2} V_{CC} = V_{BB}$$

$$R_2 = \frac{V_{CC}}{V_{BB}} \cdot R_b = \frac{9}{3,22} \cdot 964 = 2,7 \text{ k}\Omega$$

$$R_1 = 1,5 \text{ k}\Omega$$


$$(2/5) \quad R_1 \parallel R_2 = 2,7 \text{ k}\Omega \Rightarrow$$

$$3) \quad I_E' = \frac{V_{BB} - V_{BE}}{R_E} = 1,15 \text{ mA}$$

$$\varepsilon = \frac{|I_E - I_E'|}{I_E} = \frac{1,17 - 1,14}{1,14} = 0,9\%$$


0,15

4)

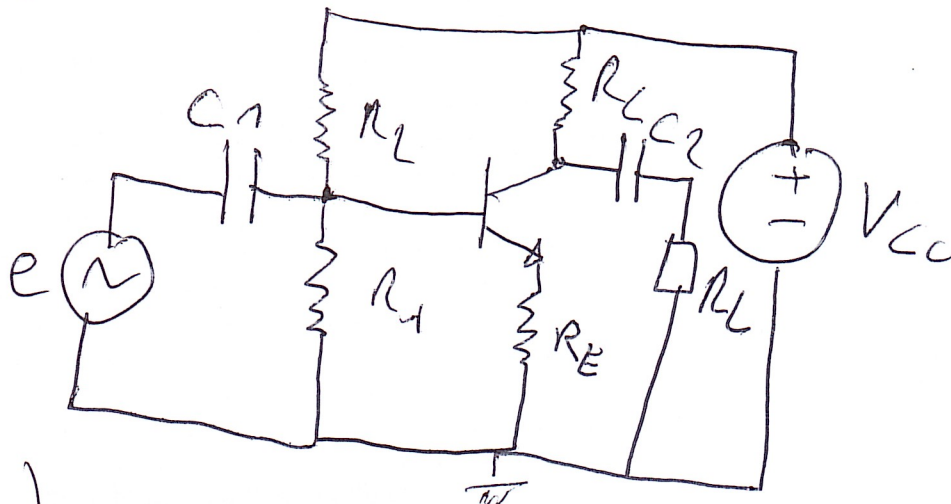

1


5)

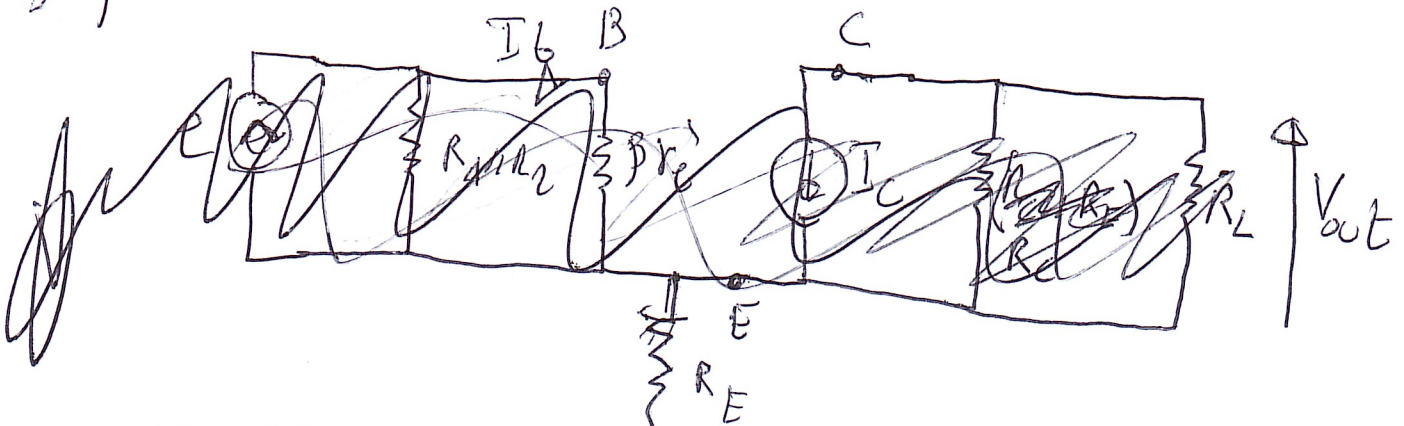

$$r_e' = \frac{25 \text{ mV}}{I_E} = \frac{25 \cdot 10^{-3} \text{ V}}{1,14 \cdot 10^{-3} \text{ A}} = 21,93 \Omega$$

0,15

6)

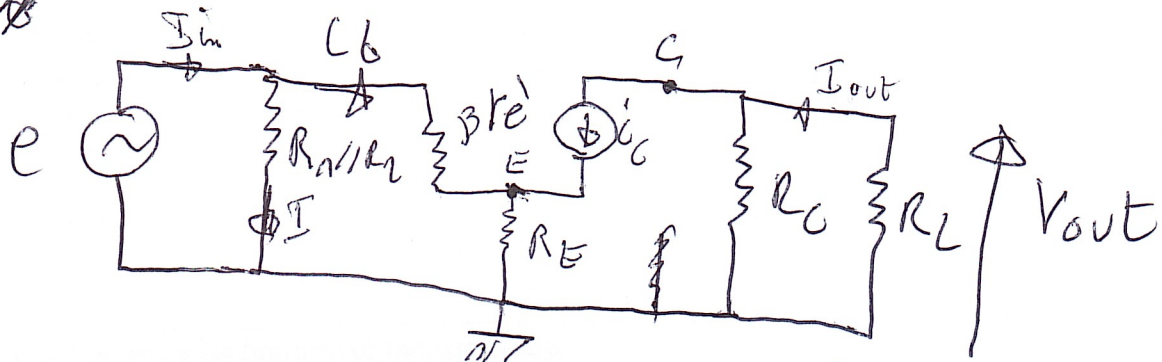

0,75

(3/5)



$$6) G_V = \frac{V_{out}}{e} \quad \left\{ \begin{array}{l} e = i_b (\beta r_e') + \beta R_E i_b \\ \approx i_E (r_e' + R_E) \end{array} \right.$$

$$G_V = - \frac{(R_L \parallel R_C)}{r_e' + R_E}$$

$$V_{out} = -(R_L \parallel R_C) I_E$$

$$G_V = -0,73$$

0,5

$$7) Z_{in} = \frac{e}{i_{in}} \quad (\text{we have } e = \beta i_b r_e' + i_e R_E)$$

$$e = i_e (r_e' + R_E)$$

$$I_{in} = I + I_b = \frac{e}{(R_1 \parallel R_2)} + \frac{I_e}{\beta}$$

$$I_{in} = \frac{e}{(R_1 \parallel R_2)} + \frac{e}{\beta (r_e' + R_E)}$$

$$I_{in} = e \left( \frac{1}{R_1 \parallel R_2} + \frac{1}{\beta (r_e' + R_E)} \right) \Rightarrow Z_{in} = \frac{e}{I_{in}} = \frac{1}{\frac{1}{R_1 \parallel R_2} + \frac{1}{\beta (r_e' + R_E)}}$$

$$Z_{in} = (R_1 \parallel R_2) \parallel (\beta (r_e' + R_E)) = 964 \parallel 2200 \approx 213$$

0,5

$$Z_{in} \approx 960 \Omega \approx (R_1 \parallel R_2)$$

$$Z_{out} = R_C \parallel R_L \parallel R_E \approx 933 \Omega$$

0,5

(4/5)

8) we have to add a capacitor in // to  $R_E$  ) ①

$$G_V \rightarrow A = \frac{R_L // R_C}{r_e'} = \frac{-1,62 \cdot 10^3}{21,93} \quad \text{) } 0,5$$
$$G_V \approx -73,9$$

$Z_{in}$  stays the same ) 0,5

$$Z_{out} = R_L // R_C \approx 1,62 \text{ k}\Omega \quad \text{) } ①$$

(5/5)