

## Chapter 4

# Sequential Circuits

1

**Dr. Iness NEDJI MILAT (Lecturer)**

[iness.nedji@ensia.edu.dz](mailto:iness.nedji@ensia.edu.dz)

**Pr. Nasreddine LAGRAA**

[Nasredine,lagraa@ensia.edu.dz](mailto:Nasredine,lagraa@ensia.edu.dz)

# Sequential vs. combinational circuit

- Combinational circuit output depends **only** on **current** inputs
- How can we design a circuit that **stores information**?
  - Use a **feedback**


- **Sequential circuit** is a **combinational** with feedbacks (**storage elements**).

- EX : **Counters** and **Shift registers**.

- Some sequential circuits may not contain combinational circuits, but only elements

- Ex : **Registers** (set of **bits**).

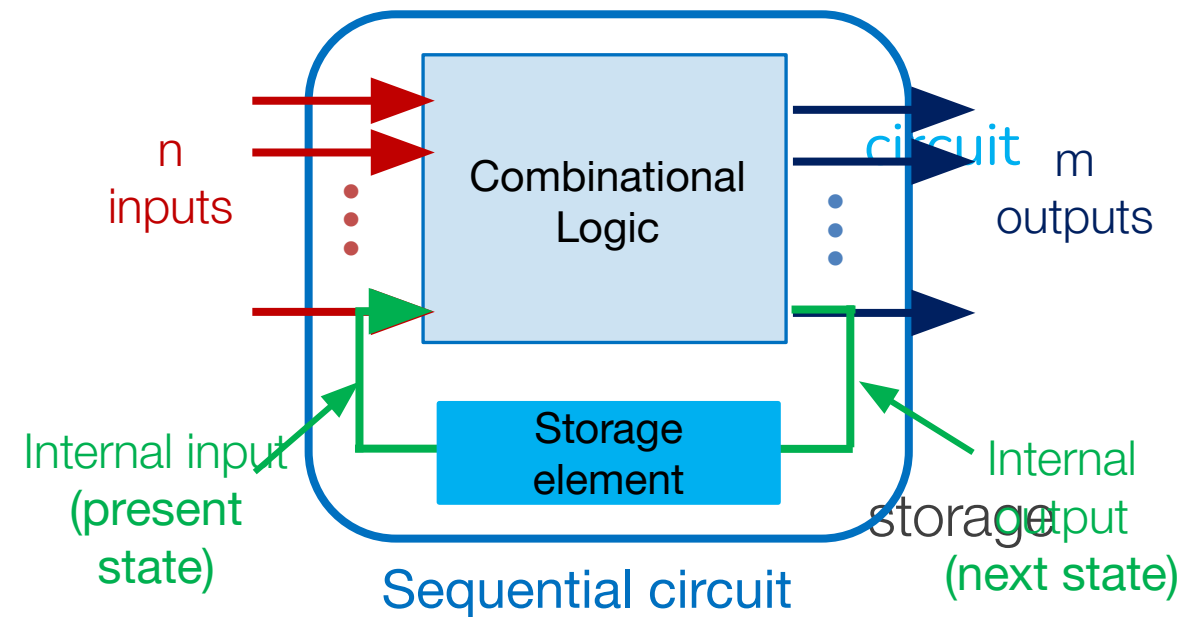- The **output** of a sequential circuit depends not only on **current inputs** but also on the **previous outputs (states)**.




## Storage elements


- Internal outputs of a sequential circuit are fed back via **storage elements**
- The **storage elements** (memory) are circuits that are capable of storing binary information.
- The binary information stored in these memory elements at any given time defines the **state** of the sequential circuit at that time.
- Each storage element memorize one bit with two states (0 or 1)
 
# Types of sequential circuits

- Sequential circuits can be Asynchronous or Synchronous.
  - **Asynchronous** sequential circuits
    - change their **states** and **output** values whenever a change in **input** values occurs.
  - **Synchronous** sequential circuits
    - change their **states** and **output** values at fixed points of time, i.e. **clock signals**. ( $\text{Clk} = 1$ )




Sequential Circuit

 

Clk 

 
# The clock

- In synchronous circuits, state values are controlled by clock signals.
  - A “clock” is a special circuit that sends electrical pulses through a circuit.
- Clocks produce electrical waveforms such as the one shown below.


 
# Clock Disciplines




- State changes occur in sequential circuits only when the clock ticks.
- Level sensitive
  - State changes when clock is high (or low)
- Edge triggered
  - State changes at clock edge



positive edge-triggered



negative edge-triggered

   



7

# Basic Storage Element

# Basic storage elements


Generally, there are two types of storage elements used: *Latches*, and *Flip-Flops*.

- **Latches** : A latch is an **asynchronous** memory element whose **excitation signals** (inputs) **control the state of the circuit**.
- A latch has two stages **Set** and **Reset**. Set input sets the output to 1. Reset input sets the output to 0.
- **Flip-flops** : A flip-flop is a **synchronous** memory element that **has clock signals control the state of the circuit**.
- Flip-flop is a latch with clock input signal



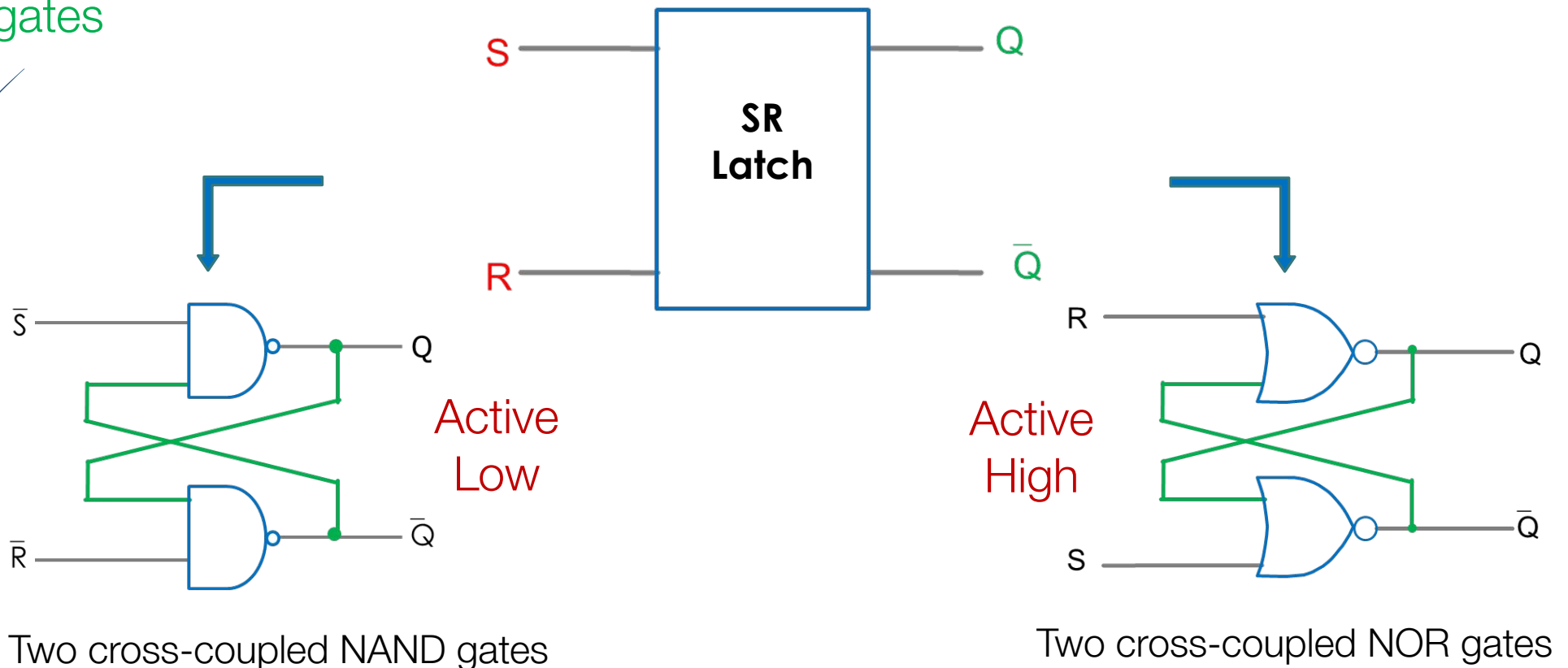
# SR Latch

- The SR latch is the basic memory element. It has two input signals ( $S$  and  $R$ ) and two outputs ( $Q$  and  $Q'$ ).
- Basic Latches can be constructed using two NAND gates or using two NOR gates



# SR Latch

Active high

 

A	B	Or	Nor
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Present state      Next state

$S$	$R$	$Q_0$	$Q$	$Q'$	Function	
0	0	0	0	1	$Q = Q_0$	Store (hold)
0	0	1	1	0	$Q = Q_0$	
0	1	0	0	1	$Q = 0$	Reset
0	1	1	0	1	$Q = 0$	
1	0	0	1	0	$Q = 1$	Set
1	0	1	1	0	$Q = 1$	
1	1	0	0	0	$Q = Q'$	Forbidden
1	1	1	0	0	$Q = Q'$	

Put 0 in bit



Put 1 in bit

To avoid


# Timing Diagram Representation

A	B	Or	Nor
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Active high

  

# SR Latch with NOR

 

		00	01	11	10
$Q(t)$ \ $SR$	0	0	0	X	1
	1	1	0	X	1

$S$	$R$	$Q_0$	$Q$	$Q'$
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	x	x
1	1	1	x	x

characteristic equation


$$Q(t+1) = S + R' Q(t)$$

Next state  
 $Q_+$

Present state  
 $Q$
 
# SR gated Latch

- Similar to the SR latch but with the extra control input EN which enables or disables the operation of the S and R inputs.
  - When  $EN=1$ , the gated SR latch operates as an SR latch.
  - When  $EN=0$ , S and R are disabled and the circuit persists in the preceding state.



EN	S	R	Q	Q <sup>+</sup>
0	x	x	0	0
0	x	x	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	x	0
1	1	0	x	1
1	1	1	x	NA

# Takeaway

## □ The fact:

- Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But,

## □ The problem:

- SR Latch has a forbidden state.

## □ Question:

- How do we avoid the forbidden state of SR Latch?

## □ Response:

- Ensure that inputs S and R are never equal to 1 at the same time,



How ?



D Latch
  
# D Latch

- D latch ensures that inputs  $S$  and  $R$  never equal to 1 at the same time.




D	Q	
0	0	1
1	1	0

$$Q^+ = Q(t+1) = D$$

- D Latch can store and change a bit like an SR Latch while avoiding the forbidden state.

 
# D Latch

- Data (D) Latch
  - Easier to use than an SR latch
  - No possibility of entering an undefined state
- When D changes, Q changes immediately (...after a delay of 1 NOT gate and 2 NORs gates)
- **SR latches** are **useful** in **control applications**
  - we often think in terms of setting or resetting a **flag** to some condition.
- **D latches** are **useful** to **store bits of information**






# D Flip-Flop (D Latch with Clock)

 

Excitation Table

CLK	D	Q	$\bar{Q}$
↑	0	0	1
↑	1	1	0

↑ : Rising Edge of Clock

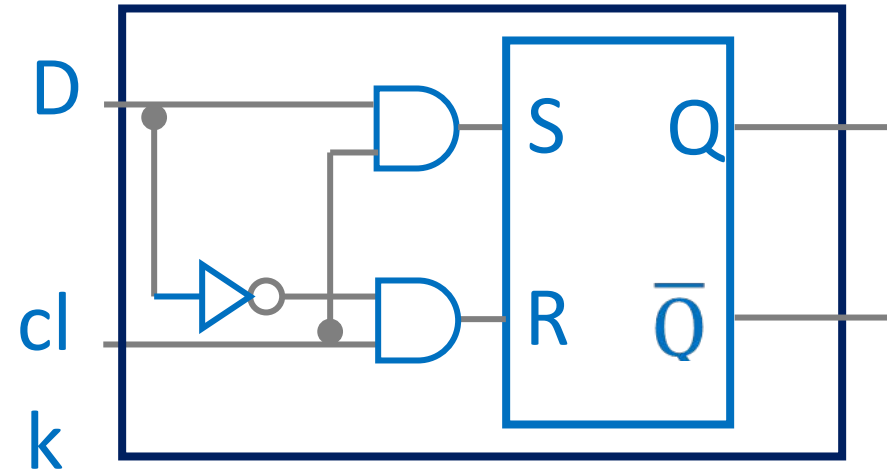

TruthTable


clk	D	Q+	
0	0	Q	}
0	1	Q	
1	0	0	1
1	1	1	0

Store bit

Reset bit

Set bit



# D Flip-Flop: Example Timing Diagram

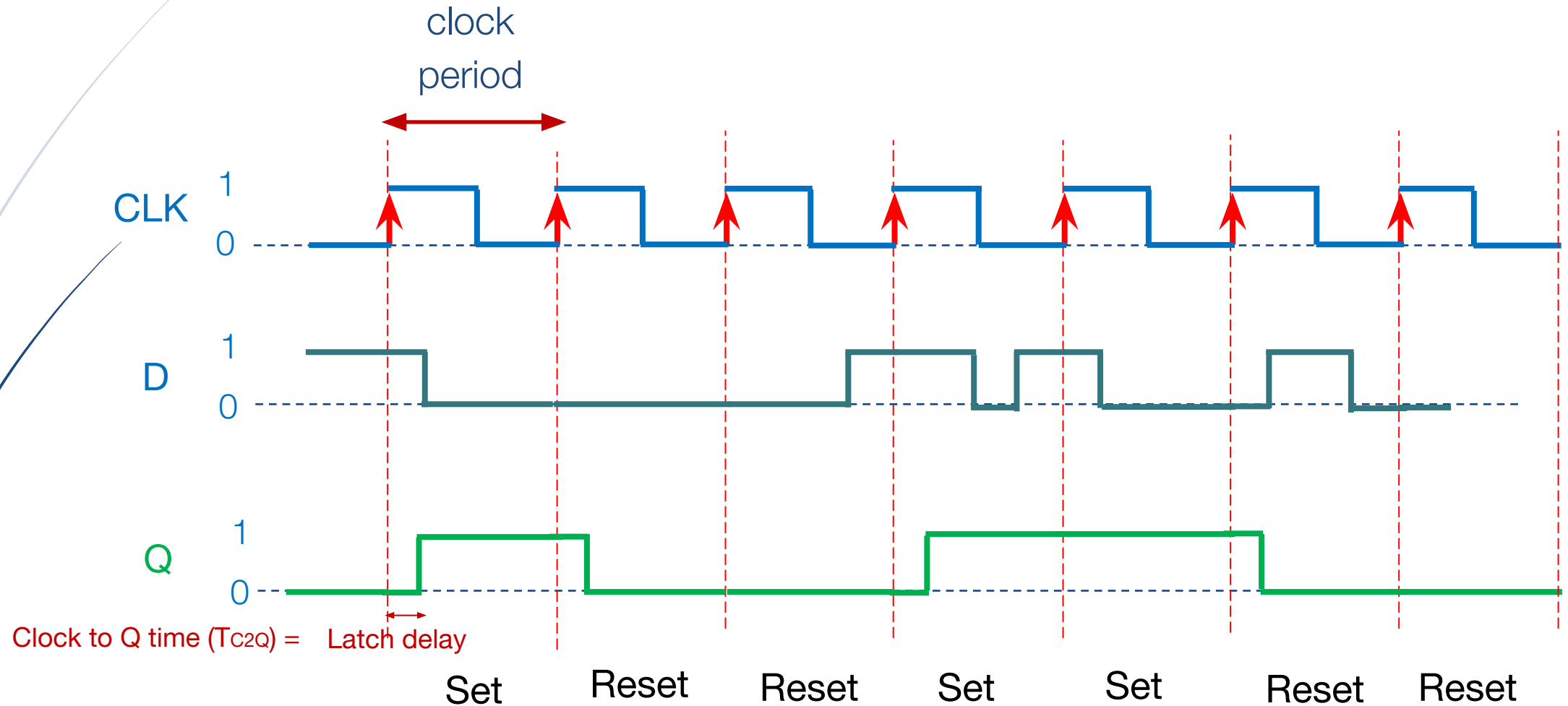

# J K Latch

- The SR latch can be modified to provide a stable state both inputs are 1 : **use JK latch.**
- The “JK” is called in honor of his inventor Jack Kilby.
- In the JK latch, the inputs J and K behave exactly like inputs S and R, But it provides a stable state when both inputs are 1 (The output is complemented).

<b>J</b>	<b>Q</b>	when
<b>K</b>	<b><math>\bar{Q}</math></b>	

 
 


J	K	Q+	
0	0	$Q_{\text{prev}}$	No change (hold /store)
0	1	0	Reset (clear)
1	0	1	Set
1	1	$\square Q$	Toggle

$$Q(t + 1) = JQ'(t) + K'Q(t)$$

# J K Flip flop


## JK Latch with clock

  

clk	J	K	Q+	
0	x	x	Q	Store
1	0	0	Q	Store
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	$\bar{Q}$	Toggle


# J/K Flip-Flop : Example Timing

J	K	Q+	
0	0	$Q_{prev}$	No change (hold /store)
0	1	0	Reset (clear)
1	0	1	Set
1	1	$\bar{Q}$	Toggle

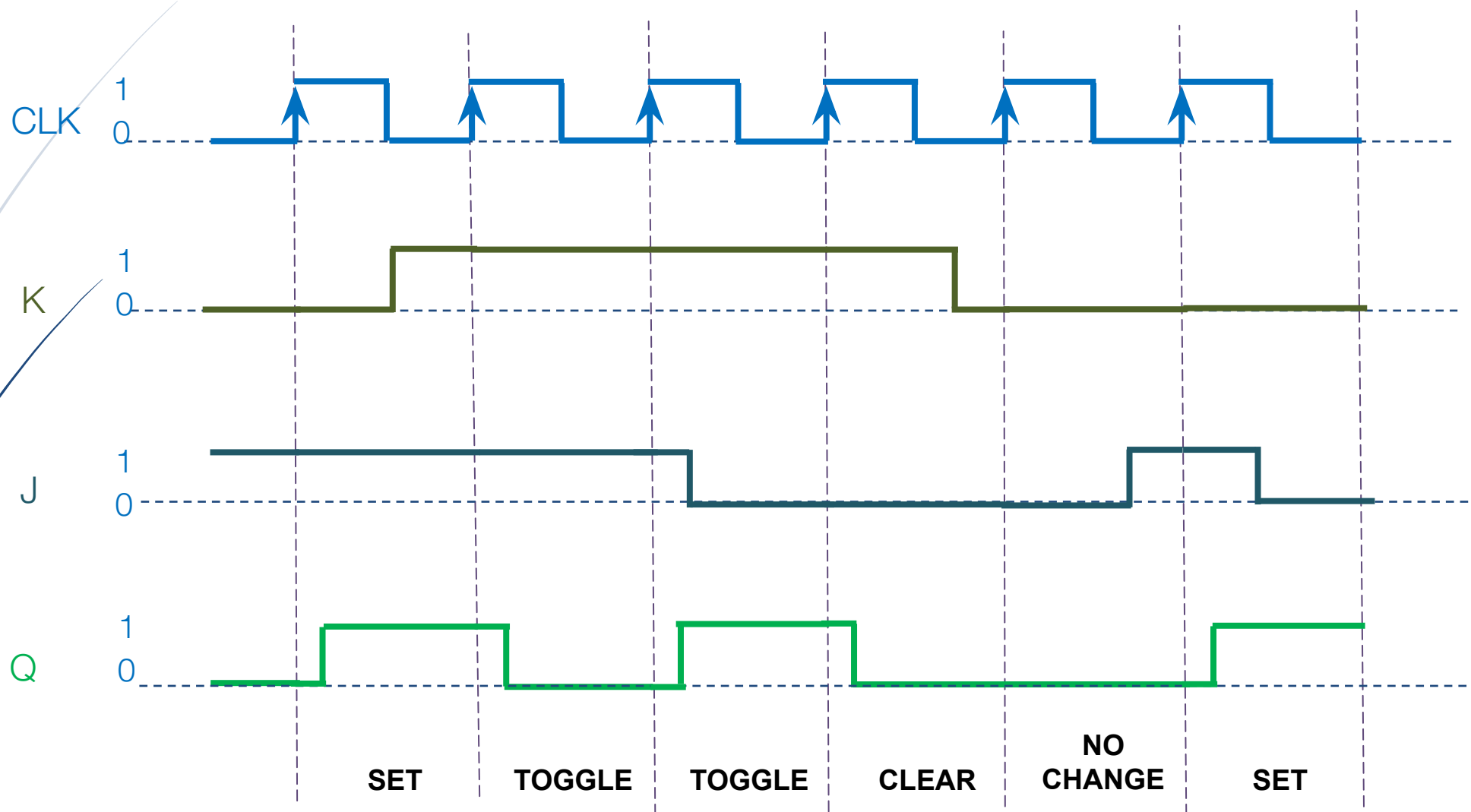
 
# T flip-flop

- T (Toggle) Flip-Flop is a complementing synchronous flip-flop.
- It can be designed using :
  - SR (Set-Reset) Flip-Flop
  - D (Data) Flip-Flop
  - JK Flip-Flop




T	Q(t+1)	
0	Q(t)	No change
1	$\overline{Q}$	Complement


$$Q(t + 1) = T \oplus Q = TQ' + T'Q$$
 
## Implementations of T flip flop

- T flip-flop can be implemented using **SR flip-flop**




 - T flip-flop can be constructed with a **D flip-flop** and a **XOR gate**.


 
## Implementations of T flip flop

- The T flip-flop can also be obtained from a **JK flip-flop** when inputs J and K are tied together.





# Characteristic Equations

SR flip-flop Characteristic Equations

$$Q(t + 1) = S + R' Q(t)$$

D flip-flop Characteristic Equations

$$Q(t + 1) = D$$

JK flip-flop Characteristic Equations


$$Q(t + 1) = JQ'(t) + K'Q(t)$$

T flip-flop Characteristic Equations

$$Q(t + 1) = T \oplus Q = TQ'(t) + T'Q(t)$$
 
# Sequential circuit timing constraints


- The Flip-Flop operates properly if the input signal (Ex: D) is stable (that is, not changing) at the time Clk goes from 0 to 1 (if rising edge). But it may lead to unpredictable results if the input signal also changes at this time.
- **Constraint 1** : the input signal **must be stable** between *setup time* and *hold time*.
  - **Setup Time ( $T_{\text{setup}}$ )**: Time duration for which the data input must be valid and stable **before** the arrival of the clock edge.
  - **Hold Time ( $T_{\text{hold}}$ )**: Time duration for which the data input must not be changed **after** the clock transition occurs.


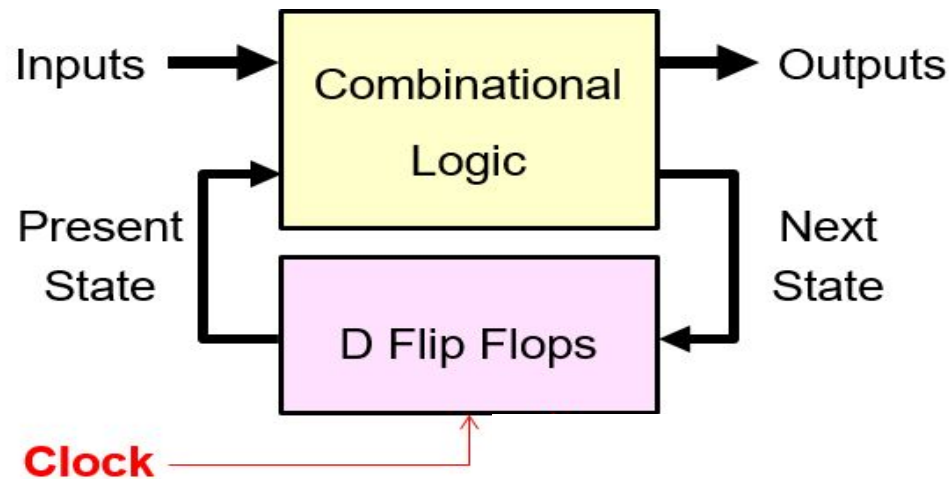
# Sequential circuit timing constraints

**Constraint 2 :** The following timing constraint is required for correct operation of the sequential circuit :

$$T_{\text{clk}} \geq T_{\text{clk2q}} + T_{\text{Combinational}} + T_{\text{setup}}$$



# Setup time violation

Timing constraint :

$$T_{\text{clk}} \geq T_{\text{clk2q}} + T_{\text{Combinational}} + T_{\text{setup}}$$

